


# **Applications Note:SY5813**

Single Stage Buck-Boost PFC Controller for LED Lighting Preliminary Specification

### **General Description**

The SY5813 is a single stage Buck-Boost PFC controller targeting at LED lighting applications. It drives the Buck-Boost converter in the Quasi-resonant mode to achieve higher efficiency. It keeps the Buck-Boost converter in constant on time operation to achieve high power factor.

## **Ordering Information**

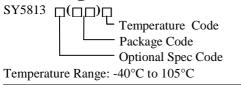


Ordering Number	Package type	Note
SY5813	SOT23-6	

### Features


- Valley turn-on of the MOSFET to achieve low switching losses
- 0.3V current sense reference voltage leads to a lower sense resistance thus a lower conduction loss.
- Internal high current MOSFET driver: 0.25A sourcing and 0.5A sinking
- Low start up current: 15µA typical
- Reliable short LED and Open LED protection
- Power factor >0.90 with single-stage conversion.
- Compact package: SOT23-6
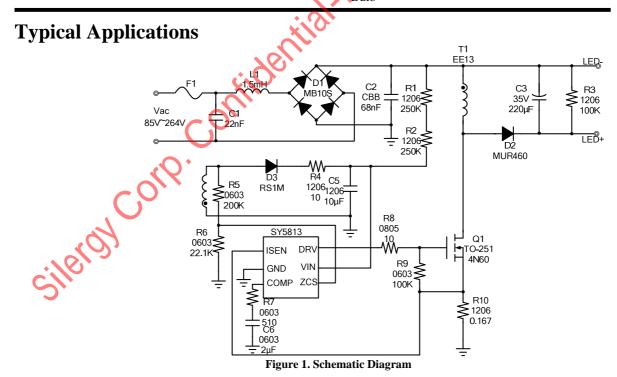
## Applications

- LED lighting
- Down light
- Tube lamp
- PAR lamp
- Bulb



1

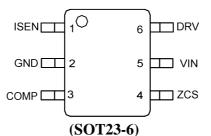

#### Top Mark: HQ for SY5813(device code: HQ, x=year code, y=week code, z= lot number code)

<b>D</b> ! 1	
Pin number	Pin Description
1	Current sense pin. Connect this pin to the source of the switch Connect the sense resistor across the source of the switch and the GND pin. (current sense resister R <sub>S</sub> : $R_{s} = k \frac{V_{REF}}{I_{OUT}}$ , k=0.167)
2	Ground pin
3	Loop compensation pin. Connect a RC network across this pin and ground to stabilize the control loop.
4	Inductor current zero-crossing detection pin. This pin receives the auxiliary winding voltage by a resister divider and detects the inductor current zero crossing point. This pin also provides over voltage protection and line regulation modification function simultaneously. If the voltage on this pin is above $V_{ZCS,OVP}$ , the IC would enter over voltage protection mode. Good line regulation can be achieved by adjusting the upper resistor of the divider.
5	Power supply pin. This pin also provides output over voltage protection along with ZCS pin.
6	Gate driver pin Connect this pin to the gate of MOSFET.
oy con	R. Court
	2 3 4 5 6






### Absolute Maximum Ratings (Note 1)

VIN, DRV	
Supply Current I <sub>VIN</sub>	30mA
ISEN, COMP	3.6V
Power Dissipation, @ TA = 25°C SOT23-6	0.6W
Package Thermal Resistance (Note 2)	
SOT23-6, θ <sub>JA</sub>	170°C/W
SOT23-6, θ <sub>JC</sub>	130°C/W
Temperature Range	45°C to 150°C
Lead Temperature (Soldering, 10 sec.)	260°C
Storage Temperature Range	

## Recommended Operating Conditions (Note 3)

VIN DRV	8V~15 4V
	01 15.11
Junction Temperature Range	40°C to 125°C
	1000 + 10500
Ambient Temperature Range	40°C to 105°C

### **Block Diagram**

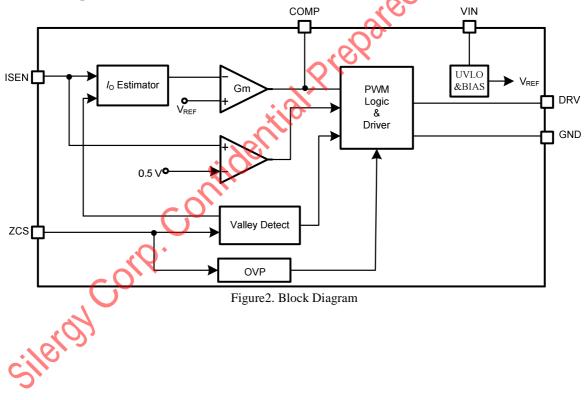



# Electrical Characteristics

 $(V_{IN} = 12V \text{ (Note 3)}, T_A = 25^{\circ}C \text{ unless otherwise specified)}$ 

Parameter	Symbol	Test Conditions	Min	Тур	Max	Unit
Power Supply Section	-			••		
Input voltage range	V <sub>VIN</sub>		8		15.4	V
VIN turn-on threshold	V <sub>VIN,ON</sub>				17.6	V
VIN turn-off threshold	V <sub>VIN,OFF</sub>		6.0		7.9	V
VIN OVP voltage	V <sub>VIN,OVP</sub>			V <sub>VIN,ON</sub> +0.85		V
Start up Current	I <sub>ST</sub>	V <sub>VIN</sub> <v<sub>VIN,OFF</v<sub>		15		μA
Operating Current	$I_{VIN}$	C <sub>L</sub> =100pF,f=15kHz		1	\$	mA
Shunt current in OVP mode	I <sub>VIN.OVP</sub>	$V_{VIN} > V_{VIN,OVP}$	1.6	2	2.5	mA
Error Amplifier Section					<b>)</b>	
Internal reference voltage	V <sub>REF</sub>		0.294	0.3	0.306	V
Current Sense Section				2		
Current limit reference voltage	V <sub>ISEN,MAX</sub>			0.5		V
ZCS pin Section			<u> </u>	)		
ZCS pin OVP voltage threshold	V <sub>ZCS,OVP</sub>		$\boldsymbol{\lambda}$	1.42		v
Gate Driver Section		<u>ا</u>	<u>S</u> 			
Gate driver voltage	V <sub>Gate</sub>			V <sub>VIN</sub>		V
Maximum source current	I <sub>SOURCE</sub>			0.25		А
Minimum sink current	I <sub>SINK</sub>			0.5		А
Max ON Time	T <sub>ON,MAX</sub>	V <sub>COMP</sub> =1.5V		24		μs
Min ON Time	T <sub>ON,MIN</sub>			400		ns
Max OFF Time	T <sub>OFF,MAX</sub>			39		μs
Min OFF Time	T <sub>OFF,MIN</sub>			2		μs
Maximum switching frequency	$\mathbf{f}_{\mathrm{MAX}}$			120		kHz
Thermal Section	•	<u>~~</u>				
Thermal Shutdown Temperature	T <sub>SD</sub>			150		°C

**Note 1**: Stresses beyond the "Absolute Maximum Ratings" may cause permanent damage to the device. These are stress ratings only. Functional operation of the device at these or any other conditions beyond those indicated in the operational sections of the specification is not implied. Exposure to absolute maximum rating conditions for extended periods may affect device reliability.

Note 2:  $\theta_{JA}$  is measured in the natural convection at  $T_A = 25$  °C on a low effective single layer thermal conductivity test board of JEDEC 51-3 thermal measurement standard. Test condition: Device mounted on 2" x 2" FR-4 substrate PCB, 2oz copper, with minimum recommended pad on top layer and thermal vias to bottom layer ground plane.

Note 3: Increase VIN pin voltage gradually higher than  $V_{VIN,ON}$  voltage then turn down to 12V.



SY5813 is a constant current Buck-Boost PFC controller targeting at LED lighting applications.

High power factor is achieved by constant on operation mode, with which the control scheme and the circuit structure are both simple.

In order to reduce the switching losses and improve EMI performance, Quasi-Resonant switching mode is applied, which means to turn on the power MOSFET at voltage valley; the start up current of SY5813 is rather small ( $15\mu$ A typically) to reduce the standby power loss further; the maximum switching frequency is clamped to 120kHz to reduce switching losses and improve EMI performance when the converter is operated at light load condition.

SY5813 provides reliable protections such as Short Circuit Protection (SCP), Open LED Protection (OLP), Over Temperature Protection (OTP), etc.


SY5813 is available with SOT23-6 package.

### **Applications Information**
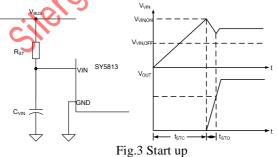
#### <u>Start up</u>

After AC supply or DC BUS is powered on, the capacitor  $C_{VIN}$  across VIN and GND pin is charged up by BUS voltage through a start up resistor  $R_{ST}$ . Once  $V_{VIN}$  rises up to  $V_{VIN-ON}$ , the internal blocks start to work.  $V_{VIN}$  will be pulled down by internal consumption of IC until the bias supply circuit could supply enough energy to maintain  $V_{VIN}$  above  $V_{VIN-OFF}$ .

The whole start up procedure is divided into two sections shown in Fig.3.  $t_{STC}$  is the  $C_{VIN}$  charged up section, and  $t_{STO}$  is the output voltage built-up section. The start up time  $t_{ST}$  composes of  $t_{STC}$  and  $t_{STO}$ , and usually  $t_{STO}$  is much smaller than  $t_{STC}$ .



The start up resistor  $R_{\text{ST}}$  and  $C_{\text{VIN}}$  are designed by rules below:

(a) Preset start-up resistor  $R_{ST}$ , make sure that the current through  $R_{ST}$  is larger than  $I_{ST}$  and smaller than  $I_{VIN\_OVP}$ 

$$\frac{V_{BUS}}{I_{VIN OVP}} < R_{ST} < \frac{V_{BUS}}{I_{ST}} (1)$$

Where  $V_{BUS}$  is the BUS line voltage.

(b) Select  $C_{VIN}$  to obtain an ideal start up time  $t_{ST}$ , and ensure the output voltage is built up at one time.

$$C_{VIN} = \frac{(\frac{V_{BUS}}{R_{ST}} - I_{ST}) \times t_{ST}}{V_{VIN_{ON}}}$$
(2)

(d) If the  $C_{VIN}$  is not big enough to build up the output voltage at one time. Increase  $C_{VIN}$  and decrease  $R_{ST}$ , go back to step (a) and redo such design flow until the ideal start up procedure is obtained.

#### Internal pre-charge design for quick start up

After  $V_{VIN}$  exceeds  $V_{VIN,ON}$ ,  $V_{COMP}$  is pre-charged by an internal current source. The PWM block won't start to output PWM signals until  $V_{COMP}$  is over the initial voltage  $V_{COMP,IC}$ , which can be programmed by  $R_{COMP}$ . Such design is meant to reduce the start up time shown in Fig.4

The voltage pre-charged  $V_{COMP\_IC}$  in start-up procedure can be programmed by  $R_{COMP}$ 

 $V_{\text{COMP_IC}} = 600 \text{mV} - 300 \mu \text{A} \times R_{\text{COMP}}$  (3)

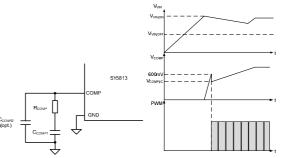


Fig.4 pre-charge scheme in start up Where  $V_{\text{COMP-IC}}$  is the pre-charged voltage of COMP pin.





Generally, a big capacitance of  $C_{COMP}$  is necessary to achieve high power factor and stabilize the system loop (1 $\mu$ F~2 $\mu$ F recommended); The voltage pre-charged in start-up procedure can be programmed by  $R_{COMP}$ ; On the other hand, larger  $R_{COMP}$  can provide larger phase margin for the control loop; A small ceramic capacitor is added to suppress high frequency interruption (10pF~100pF is recommended if necessary)

#### Shut down

After AC supply or DC BUS is powered off, the energy stored in the BUS capacitor will be discharged. When the auxiliary winding of Buck-Boost inductor can not supply enough energy to VIN pin,  $V_{VIN}$  will drop down. Once  $V_{VIN}$  is below  $V_{VIN-OFF}$ , the IC will stop working and  $V_{COMP}$  will be discharged to zero.

#### **Constant-current control**

The switching waveforms are shown in Fig.5.

The output current  $I_{OUT}$  can be represented by,

$$I_{OUT} = \frac{I_{PK}}{2} \times \frac{t_{DIS}}{t_s} (4)$$

Where  $I_{PK}$  is the peak current of the inductor;  $t_{DIS}$  is the discharge time of Buck-Boost inductor;  $t_S$  is the switching period.

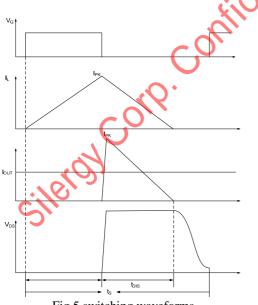


Fig.5 switching waveforms

The inductor peak current  $I_{PK}$  and inductor current discharge time  $t_{DIS}$  can be detected by the IC, and the effect of the leakage inductor can be compensated by internal control scheme.  $I_{OUT}$  can be induced finally by

$$I_{OUT} = \frac{k_1 \times k_2 \times V_{REF}}{R_s} (5)$$

Where  $k_1$  is the output current weight coefficient;  $k_2$  is the output modification coefficient;  $V_{REF}$  is the internal reference voltage;  $R_S$  is the current sense resistor.

 $k_1$ ,  $k_2$  and  $V_{REF}$  are all internal constant parameters,  $I_{OUT}$  can be programmed by  $R_s$ .



#### Quasi-Resonant Operation

QR mode operation provides low turn-on switching losses for Buck-Boost converter.

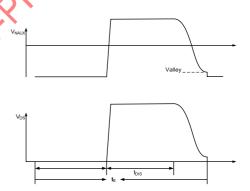


Fig.6 QR mode operation

The voltage across drain and source of the MOSFET is reflected by the auxiliary winding of the Buck-Boost inductor. ZCS pin detects the voltage across the auxiliary winding by a resistor divider. When the voltage across drain and source of the MOSFET is at voltage valley, the MOSFET would be turned on.

Over Voltage Protection (OVP) & Open LED Protection (OLP)

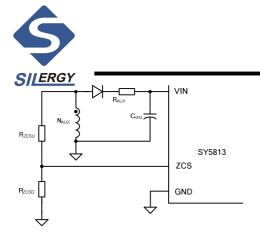


Fig.7 Bias current is supplied by auxiliary winding

The output voltage is reflected by the auxiliary winding voltage of the Buck-Boost inductor, and both ZCS pin and VIN pin provide over voltage protection function. When the load is null or large transient happens, the output voltage will exceed the rated value. When  $V_{VIN}$  exceeds  $V_{VIN,OVP}$  or  $V_{ZCS}$  exceeds  $V_{ZCS,OVP}$ , the over voltage protection is triggered and the PWM output will be stopped. Then  $V_{VIN}$  is discharged by an internal current source  $I_{VIN,OVP}$ . Once  $V_{VIN}$  is below  $V_{VIN,OFF}$ , the IC will shut down and be charged again by BUS voltage through start up resistor. If the over voltage condition still exists, the system will operate in hiccup mode.

Thus, the turns of the auxiliary winding  $N_{AUX}$  and the resistor divider is related with the OVP function.

$$\frac{V_{ZCS\_OVP}}{V_{OVP}} = \frac{N_{AUX}}{N} \times \frac{R_{ZCSD}}{R_{ZCSU} + R_{ZCSD}} (7)$$

$$\frac{V_{VIN\_OVP}}{V_{OVP}} \ge \frac{N_{AUX}}{N} (8)$$

Where  $V_{OVP}$  is the output over voltage specification;  $R_{ZCSU}$  and  $R_{ZCSD}$  compose the resistor divider. The turns ratio of N to  $N_{AUX}$  and the ratio of  $R_{ZCSU}$  to  $R_{ZCSD}$  could be induced from equation (7) and (8).

#### Short Circuit Protection (SCP)

When the output is shorted to ground, the output voltage is clamped to zero. The voltage of the auxiliary winding is proportional to the output winding, so  $V_{VIN}$  will drop down without auxiliary winding supply. Once  $V_{VIN}$  is below  $V_{VIN,OFF}$ , the IC will shut down and be charged again by the BUS voltage through the start up resistor. If the short circuit condition still exists, the system will operate in hiccup mode. In order to guarantee SCP function not effected by voltage spike of auxiliary winding, a filter resistor  $R_{AUX}$  is needed (10 $\Omega$  typically) shown in Fig.7.

#### Line regulation modification

The IC provides line regulation modification function to improve line regulation performance.

Due to the sample delay of ISEN pin and other internal delay, the output current increases with increasing input BUS line voltage. A small compensation voltage  $\Delta V_{ISEN-C}$  is added to ISEN pin during ON time to improve such performance. This  $\Delta V_{ISEN-C}$  is adjusted by the upper resistor of the divider connected to ZCS pin.

$$\Delta V_{\text{ISEN,C}} = V_{\text{BUS}} \times \frac{N_{\text{AUX}}}{N} \times \frac{1}{R_{\text{ZCSU}}} \times k_3 (9)$$

Where  $R_{ZCSU}$  is the upper resistor of the divider; k3 is an internal constant as the modification coefficient.

The compensation is mainly related with  $R_{ZCSU}$ , larger compensation is achieved with smaller  $R_{ZCSU}$ . Normally,  $R_{ZCS}$  ranges from  $100k\Omega \sim 10M\Omega$ .

Then R<sub>ZCSD</sub> can be selected by,

$$\frac{\frac{V_{ZCS_{OVP}}}{V_{OUT}} \times \frac{N}{N_{AUX}}}{1 - \frac{V_{ZCS_{OVP}}}{V_{OUT}} \times \frac{N}{N_{AUX}}} \times R_{ZCSU} > R_{ZCSD} (10),$$

And,

$$R_{zCSD} \ge \frac{\frac{V_{ZCS_{OVP}}}{V_{OVP}} \times \frac{N}{N_{AUX}}}{1 - \frac{V_{ZCS_{OVP}}}{V_{OVP}} \times \frac{N}{N_{AUX}}} \times R_{zCSU} (11)$$

Where  $V_{OVP}$  is the output over voltage protection specification;  $V_{OUT}$  is the rated output voltage;  $R_{ZCSU}$  is the upper resistor of the divider; N and  $N_{AUX}$  are the turns of main winding and auxiliary winding separately.

### **Power Device Design**

#### **MOSFET and Diode**

When the operation condition is with maximum input voltage and full load, the voltage stress of MOSFET and output power diode is maximized;

7





 $V_{\text{MOS}\_DS\_MAX} = \sqrt{2} V_{\text{AC}\_MAX} + V_{\text{OUT}} (12)$  $V_{\text{D}\_R\_MAX} = \sqrt{2} V_{\text{AC}\_MAX} + V_{\text{OUT}} (13)$ Where V are is maximum in

Where  $V_{AC,MAX}$  is maximum input AC RMS voltage;  $V_{OUT}$  is the rated output voltage; When the operation condition is with minimum input voltage and full load, the current stress of MOSFET and power diode is maximized.

 $I_{\text{MOS}\_PK\_MAX} = I_{L\_PK\_MAX} (14)$  $I_{D AVG} = I_{OUT} (15)$ 

Where  $I_{L\mbox{-}PK\mbox{-}MAX}$  is maximum inductor peak current, which will be introduced later.

#### Inductor (L)

In Quasi-Resonant mode, each switching period cycle  $t_s$  consists of three parts: current rising time  $t_1$ , current falling time  $t_2$  and qµAsi-resonant time  $t_3$  shown in Fig.8.

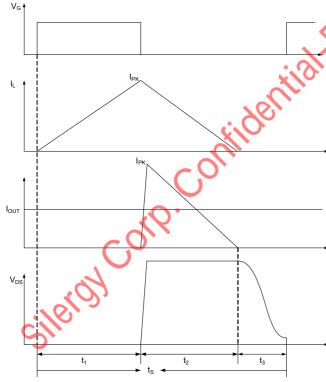


Fig.8 switching waveforms

The system operates in the constant on time mode to achieve high power factor. The ON time increases with the input AC RMS voltage decreasing and the load increasing. When the operation condition is with minimum input AC RMS voltage and full load, the ON time is maximized. On the other hand, when the input voltage is at the peak value, the OFF time is maximized. Thus, the minimum switching frequency  $f_{S-MIN}$  happens at the peak value of input voltage with minimum input AC RMS voltage and maximum load condition; Meanwhile, the maximum peak current through MOSFET and the transformer happens.

Once the minimum frequency  $f_{S-MN}$  is set, the inductance of the transformer could be induced. The design flow is shown as below:

(a) Preset minimum frequency f<sub>S-MIN</sub>

(b) Compute relative  $t_s$ ,  $t_1$  ( $t_3$  is omitted to simplify the design here)

$$t_{s} = \frac{1}{f_{s,MIN}} (16)$$

$$t_{1} = \frac{1}{\sqrt{2}V_{AC_{MIN}} + V_{OUT} + V_{D_{c}F}} (17)$$

(c) Design inductance L

$$L = \frac{V_{AC\_MIN}^2 \times t_1^2 \times \eta}{2P_{OUT} \times t_s} (18)$$

(d) Compute t<sub>3</sub>

$$t_3 = \pi \times \sqrt{L \times C_{\text{Drain}}}$$
 (19)

Where  $C_{\text{Drain}}$  is the parasitic capacitance at drain of MOSFET.

(e) Compute inductor maximum peak current  $I_{L\text{-}PK\text{-}MAX}$  and RMS current  $I_{L\text{-}RMS\text{-}MAX}$  for the transformer fabrication.

$$I_{L_{PK}MAX} = \frac{2P_{OUT} \times \left[\frac{L}{\sqrt{2}V_{AC_{MIN}}} + \frac{L}{V_{OUT} + V_{D_{F}}}\right]}{L \times \eta}$$
$$+ \frac{\sqrt{4P_{OUT}^{2} \times \left(\frac{L}{\sqrt{2}V_{AC_{MIN}}} + \frac{L}{V_{OUT} + V_{D_{F}}}\right)^{2} + 4L \times \eta \times P_{OUT} \times t_{3}}}{L \times \eta}$$

(20)

Where  $\eta$  is the efficiency; P<sub>OUT</sub> is rated full load power

\$

Adjust  $t_1$  and  $t_s$  to  $t_1'$  and  $t_s'$  considering the effect of  $t_3$  $t'_s = \frac{\eta \times L \times I^2_{L_PK_MAX}}{4P_{OUT}} (21)$ 

$$t_{1}^{\prime} = \frac{L \times I_{L\_PK\_MAX}}{\sqrt{2}V_{AC\_MIN}} (22)$$

$$\mathbf{I}_{\mathrm{L}_{\mathrm{RMS}_{\mathrm{MAX}}}} \approx \sqrt{\frac{1}{6}} \times \mathbf{I}_{\mathrm{L}_{\mathrm{PK}_{\mathrm{MAX}}}} (23)$$

 $t_2 = t_s - t_1 - t_s (24)$ (f) Compute RMS current  $I_{L-RMS-MAX}$  of the MOSFET

$$I_{\text{MOS}\_\text{RMS}\_\text{MAX}} \approx \sqrt{\frac{t_1'}{6t_s'}} \times I_{\text{L}\_\text{PK}\_\text{MAX}} (25)$$

#### Inductor design (N, N<sub>AUX</sub>)

The design of the inductor is similar with ordinary Buck-Boost inductor. the parameters below are necessary:

Necessary parameters	
Inductance	L
inductor maximum current	I <sub>L-PK-MAX</sub>
Inductor maximum RMS current	I <sub>L-RMS-MAX</sub>

The design rules are as followed:

(a) Select the magnetic core style, identify the effective area  $A_{e}$ .

(b) Preset the maximum magnetic flux

ΔB=0.22~0.26T

(c) Compute inductor turn N

$$N = \frac{L \times I_{L_{PK}MAX}}{\Delta B \times A_{e}} (26)$$

(e) compute auxiliary turn N<sub>AUX</sub>

$$N_{AUX} = N \times \frac{V_{VIN}}{V_{OUT}}$$
 (27)

Where  $V_{\text{VIN}}$  is the working voltage of VIN pin (10V~11V is recommended).


(f) Select an appropriate wire diameter

With  $I_{L-RMS-MAX}$ , select appropriate wire to make sure the current density ranges from  $4A/mm^2$  to  $10A/mm^2$ .

(g) If the winding area of the core and bobbin is not enough, reselect the core style, go to (a) and redesign the transformer until the ideal transformer is achieved.
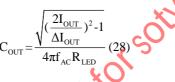
#### **Output Capacitor Cout**

Preset the output current ripple  $\Delta I_{OUT}$  Cour is induced by



Where  $I_{OUT}$  is the rated output current;  $\Delta I_{OUT}$  is the demanded current ripple;  $f_{AC}$  is the input AC supply frequency;  $R_{LED}$  is the equivalent series resistor of the LED load

## Layout

(a) To achieve better EMI performance and reduce line frequency ripples, the output of the bridge rectifier should be connected to the BUS line capacitor first, then to the switching circuit.

(b) The ground of the BUS line capacitor, the ground of the current sample resistor and the signal ground of the IC should be connected in a star connection.

(c) The circuit loop of all switching circuit should be kept small.

(d) The wire connected to ISEN and DRV should be as thick as possible.

(e) The resistor divider is recommended to be put beside the IC.





A design example of typical application is shown below step by step.

#1. Identify design specification

Design Specification			
V <sub>AC</sub> (RMS)	85V~264V	V <sub>OUT</sub>	24V
I <sub>OUT</sub>	300mA	η	90%

#2. Transformer design (L)

Conditions			- vSi
V <sub>AC,MIN</sub>	85V	V <sub>AC-MAX</sub>	264V
V <sub>MOS_DS_MAX_</sub>	600V	V <sub>D,F</sub>	1V
P <sub>OUT</sub>	7.2W	f <sub>S-MIN</sub>	50kHz
C <sub>Drain</sub>	100pF		
$V = \sqrt{2}V$	$+V = \sqrt{2} \times 264 + 24 -$	-397 3V	2
$V_{MOS DS MAX} = \sqrt{2} V_{AC}$	$_{MAX} + V_{OUT} = \sqrt{2} \times 264 + 24 =$	-397.3V	<i>2</i>
	$_{MAX} + V_{OUT} = \sqrt{2} \times 264 + 24 =$	-397.3V	S <sub>S/1</sub>
$V_{MOS_{DS_{MAX}}} = \sqrt{2} V_{AC_{AC_{AC_{AC_{AC_{AC_{AC_{AC_{AC_{AC$	$_{\rm MAX} + V_{\rm OUT} = \sqrt{2} \times 264 + 24 =$	-397.3V	, 2 <sup>21</sup>

$$V_{MOS_{DS_{MAX}}} = \sqrt{2} V_{AC_{MAX}} + V_{OUT} = \sqrt{2} \times 264 + 24 = 397.3 V_{MOS_{MAX}} + V_{OUS_{MAX}} + V_{OUS_{MAX}} + V_{OUS_{MAX}} + V_{OU$$

(c) Compute the switching period  $t_s$  and ON time  $t_1$  at the peak of input voltage.

$$t_{s} \!=\! \frac{1}{f_{s\_MIN}} \!=\! 20 \mu s$$

$$t_{1} = \frac{t_{s} \times (V_{OUT} + V_{D_{L}F})}{\sqrt{2}V_{AC_{MIN}} + V_{OUT} + V_{D_{L}F}} = \frac{20\mu s \times (24V + 1V)}{\sqrt{2} \times 85V + 24V + 1V} = 3.44\mu s$$

(d) Compute the inductance L

$$L = \frac{V_{AC_{MIN}}^2 \times t_s^2 \times \eta}{2P_{0TT} \times t_s} = \frac{85V^2 \times 3.44\mu s^2 \times 0.9}{2 \times 7.2W \times 20\mu s} = 267\mu H$$
  
Set  
$$L = 300\mu H$$

(e) Compute the Quasi-Resonant time t<sub>3</sub>

$$t_3 = \pi \times \sqrt{L \times C_{\text{Drain}}} = \pi \times \sqrt{300 \mu H \times 100 p F} = 544 \text{ ns}$$

(f) Compute inductor maximum peak current I<sub>L-PK-MAX</sub>

$$I_{L_{PK,MAX}} = \frac{2P_{OUT} \times [\frac{L}{\sqrt{2}V_{AC,MIN}} + \frac{L}{(V_{OUT} + V_{D,P})}]}{L \times \eta} + \frac{\sqrt{4P_{OUT}^2 \times [\frac{L}{\sqrt{2}V_{AC,MIN}} + \frac{L}{V_{OUT} + V_{D,P}}]^2 + 4L \times \eta \times P_{OUT} \times t_3}}{L \times \eta} = 1.583A$$
Adjust switching period ts and ON time t<sub>1</sub> to t's and t'<sub>1</sub>.
$$t'_{5} = \frac{\eta \times L \times I_{L,PK,MAX}^2}{4P_{OUT}} = \frac{0.9 \times 300 \mu H \times 1.583A^2}{4 \times 7.2W} = 23.5 \mu s$$
Compute inductor maximum RMS current I<sub>L-RMS,MAX</sub>

$$t'_{1} = \frac{L \times I_{L,PK,MAX}}{\sqrt{2}V_{AC,MIN}} = \frac{300 \mu H \times 1.583A}{\sqrt{2} \times 85V} = 3.95 \mu s$$
Compute inductor maximum RMS current I<sub>L-RMS,MAX</sub>

$$I_{L,RMS,MAX} \approx \sqrt{\frac{1}{6}} \times I_{L,PK,MAX} = \sqrt{\frac{1}{6}} \times 1.583A = 0.646A$$
(g) Compute RMS current I<sub>L-RMS,MAX</sub> of the MOSFET
$$I_{MOS,RMS,MAX} = \sqrt{\frac{1'_{1}}{6t'_{5}}} \times I_{L,PK,MAX} = \sqrt{\frac{3.95 \mu s}{6 \times 23.5 \mu s}} \times 1.583A = 0.265A$$

$$t'_{2} = t_{5} \cdot t_{1} \cdot t_{5} = 2.5 \mu s - 3.95 \mu s - 5.44 \mu s = 19 \mu s$$
#3. Select power MOSFET and output power diode
Refer to Power Device Design
$$\frac{Known conditions at this step}{V_{AC,MAX}} = \frac{264V}{24V} \qquad \eta = \frac{90\%}{1V}$$

(a) Compute the voltage and the current stress of MOSFET:

$$V_{MOS\_DS\_MAX} = \sqrt{2} V_{AC\_MAX} + Y_{OUT} + V_{D\_F}$$
$$= \sqrt{2} \times 264V + 24V + 1V$$
$$= 398.4V$$
$$I_{MOS\_PK\_MAX} = I_{L\_PK\_MAX} = 1.583A$$
$$I_{MOS\_RMS\_MAX} = 0.265A$$

(b) Compute the voltage and the current stress of power diode

$$V_{D_{D_{AC}MAX}} = \sqrt{2}V_{AC_{MAX}} + V_{OUT} = \sqrt{2} \times 264V + 24V = 397.4V$$



 $I_{D\_AVG} \!=\! I_{OUT} \!=\! 0.3A$ 

#4. Select the output capacitor  $C_{\mbox{\scriptsize OUT}}$ 

Refer to Power Device Design

Conditions			
I <sub>OUT</sub>	300mA	$\Delta I_{OUT}$	I <sub>OUT</sub>
f <sub>AC</sub>	50Hz	R <sub>LED</sub>	7×1.6Ω
The output capacitor is			soth
$C_{OUT} = \frac{\sqrt{\left(\frac{2I_{OUT}}{\Delta I_{OUT}}\right)^2 - 1}}{4\pi f_{AC}R_{LED}} = \frac{1}{4\pi}$	$\frac{\sqrt{(\frac{2\times0.3A}{0.3A})^2 - 1}}{\pi \times 50 \text{Hz} \times 7 \times 1.6 \Omega} = 246 \mu \text{F}$	.0	I <sub>OUT</sub> 7×1.6Ω 50 7×1.6Ω 264V×1.414
#5. Set VIN pin		A	5
Refer to Start up		ret	
Conditions		<u> </u>	
V <sub>BUS-MIN</sub>	85V×1.414	V <sub>BUS-MAX</sub>	264V×1.414
I <sub>ST</sub>	15µA (typical)	VIN-ON	16V (typical)
I <sub>VIN-OVP</sub>	2m A (typical)		500ms (designed by user)
(a) $R_{ST}$ is preset $R_{ST} < \frac{V_{BUS}}{I_{ST}} = \frac{85V \times 1.414}{15\mu A}$	==8.01MQ,	7	
$R_{ST} > \frac{V_{BUS}}{I_{VIN_{OVP}}} = \frac{264V \times 1}{2mA}$ Set R <sub>ST</sub>	.414 186kΩ		
$R_{ST} = 250k\Omega \times 2 = 500k\Omega$ <b>(b)</b> Design C <sub>VIN</sub>			
$C_{VIN} = \frac{\left(\frac{V_{BUS}}{R_{ST}} - I_{ST}\right) \times t_{ST}}{V_{VIN ON}} =$	$(\frac{85V\times1.414}{500k\Omega}-15\mu A)\times500$	ms	

Set  $C_{\text{VIN}}$ 



 $C_{_{VIN}}{=}10\mu F$ 

#6 Set COMP pin

#### Refer to Internal pre-charge design for quick start up

Parameters designed			
R <sub>COMP</sub>	510Ω	V <sub>COMP,IC</sub>	600mV
C <sub>COMP1</sub>	2µF	C <sub>COMP2</sub>	0

#### Refer to Constant-current control

COMP1	2μ1*	CCOMP2	0
	ense resistor to achieve id ant-current control	leal output current	coty sin
Known condition	ons at this step		
$k_1 \times k_2$	0.167	I <sub>OUT</sub>	0.3A
V <sub>REF</sub>	0.3V		
The current sen	se resistor is		
$R_{s} = \frac{k_{1} \times k_{2} \times V}{I_{OUT}}$	$\frac{0.167 \times 0.3V}{0.3A} = 0.167$	Ω	, Pale
#9 set ZCS pin		· · · ·	
Refer to Line re	egulation modification a	nd Over Voltage Protection	(OVP) & Open Loop Protection (


$$R_{s} = \frac{k_{1} \times k_{2} \times V_{REF}}{I_{OUT}} = \frac{0.167 \times 0.3V}{0.3A} = 0.167\Omega$$

# Refer to Line regulation modification and Over Voltage Protection (OVP) & Open Loop Protection (OLP)

First identify R <sub>ZCSU</sub> need for line regulation.	2


Known conditions at this	step			
Parameters Designed		$\sim$		
R <sub>ZCSU</sub>	200KQ			

Then compute $R_{ZCSU}$ $\bigwedge$		
Conditions		
V <sub>ZCS_OVP</sub>	V <sub>OVP</sub>	30V
V <sub>OUT</sub>		
Parameters designed		
$R_{ZCSD}$ 22.1k $\Omega$		

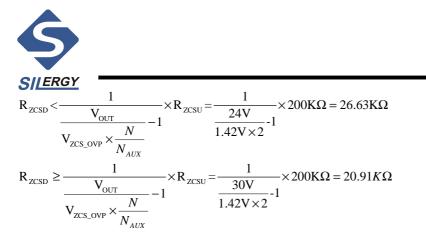

$$R_{zcsp} = 22.1 k\Omega$$


#10 final result

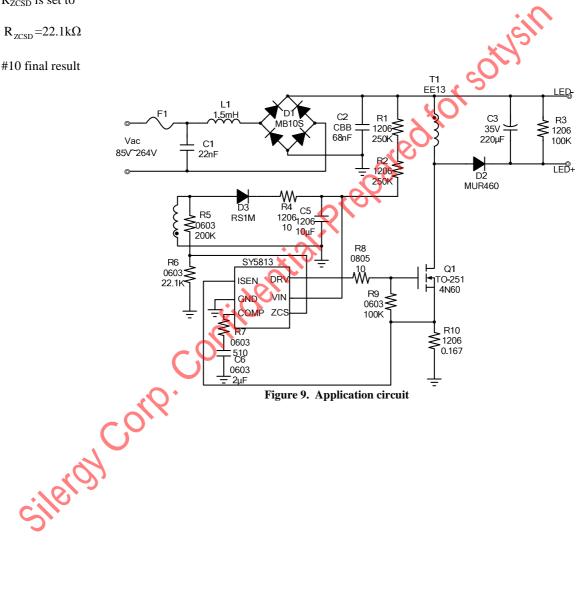

SY5813



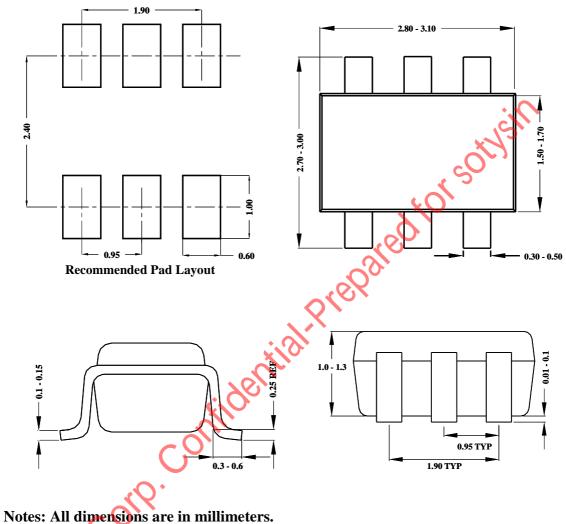SOT23-6 Package outline & PCB layout design



All dimensions don't include mold flash & metal burr.

sile



## **Taping & Reel Specification**

1. Taping orientation

SOT23-6

